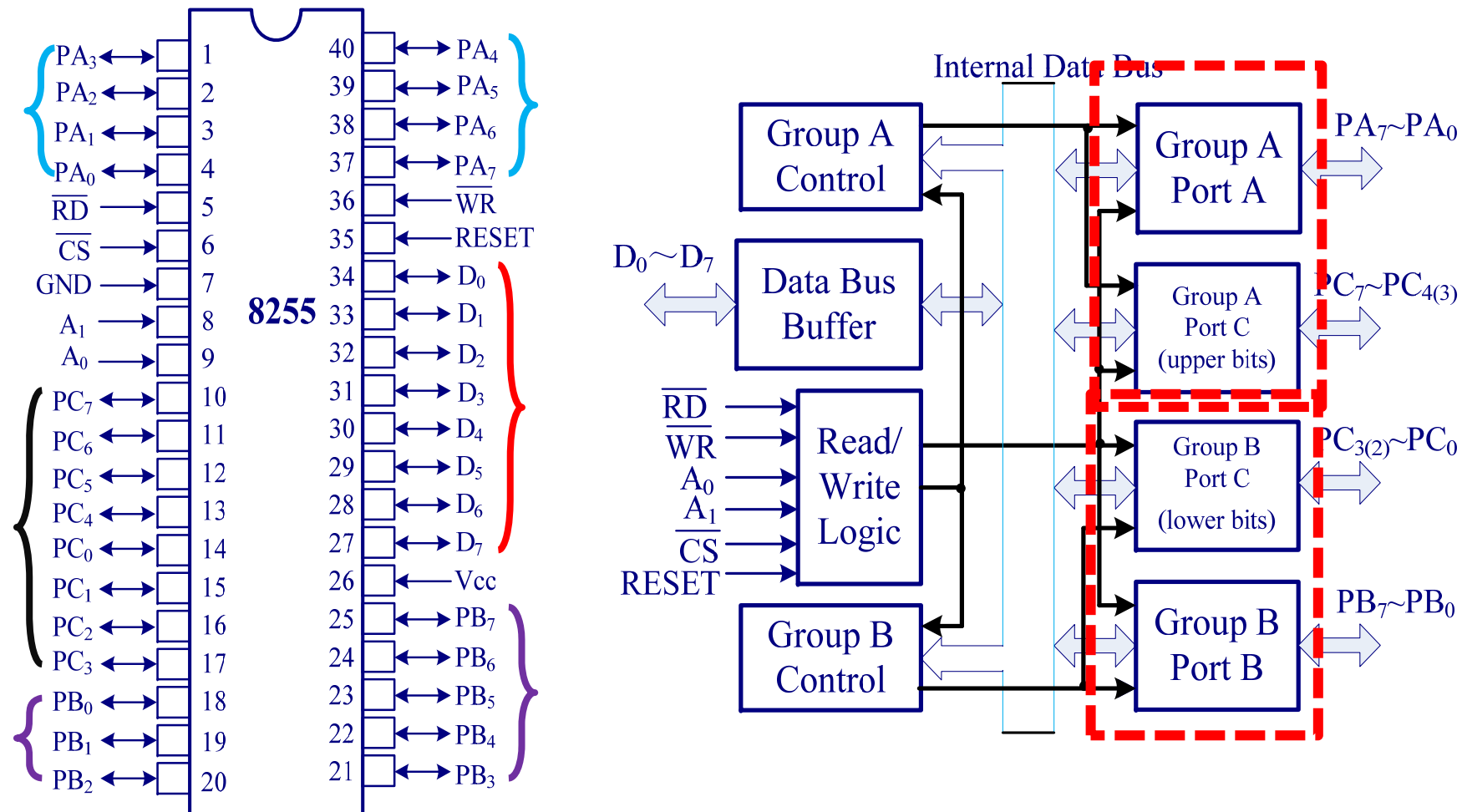


Lecture 8: 8255 PPI Chip

The 80x86 IBM PC and Compatible Computers

Chapter 11.4
8255 PPI Chip

Package & Internal Structure



Internal Structure and Pins

⌘ Three data ports: A, B, and C

- ☒ Port A ($PA_0 \sim PA_7$): can be programmed **all** as input/output
- ☒ Port B ($PB_0 \sim PB_7$): can be programmed **all** as input/output
- ☒ Port C ($PC_0 \sim PC_7$): can be split into two separate parts *PCU* and *PCL*; any bit can be programmed **individually**

⌘ Control register (CR)

- ☒ Internal register: used to setup the chip

⌘ Group A, Group B and control logic

- ☒ Group A (PA & PCU)
- ☒ Group B (PB & PCL)

Internal Structure and Pins

⌘ Data bus buffer

- ☒ An interface between CPU and 8255
- ☒ Bidirectional, tri-state, 8-bit

⌘ Read/Write control logic

- ☒ Internal and external control signals
- ☒ **RESET**: high-active, clear the control register, all ports are set as input port
- ☒ **~CS**, **~RD**, **~WR**
- ☒ **A₁**, **A₀**: port selection signals

~CS	A ₁	A ₀	~RD	~WR	Function
0	0	0	0	1	PA->Data bus
0	0	1	0	1	PB->Data bus
0	1	0	0	1	PC->Data bus
0	0	0	1	0	Data bus->PA
0	0	1	1	0	Data bus->PB
0	1	0	1	0	Data bus->PC
0	1	1	1	0	Data bus->CR
1	×	×	1	1	D ₀ ~D ₇ in float

Operation Modes

⌘ Input/output modes

☒ Mode 0, simple I/O mode:

☒ **PA, PB, PC**: $PCU\{PC_4 \sim PC_7\}$, $PCL\{PC_0 \sim PC_3\}$

☒ No **Handshaking**: *negotiation between two entities before communication*

☒ Each port can be programmed as input/output port

☒ Mode 1:

☒ **PA, PB** can be used as input/output ports with *handshaking*

☒ $PCU\{PC_3 \sim PC_7\}$, $PCL\{PC_0 \sim PC_2\}$ are used as handshake lines for PA and PB, respectively

☒ Mode 2:

☒ Only **PA** can be used for *bidirectional handshake* data transfer

☒ $PCU\{PC_3 \sim PC_7\}$ are used as handshake lines for PA

⌘ Bit set/reset (BSR) mode

☒ Only **PC** can be used as output port

☒ Each line of PC can be set/reset individually

Control Register & Op. Modes

⌘ Control Register

- ⏏ A 8-bit internal register in 8255
- ⏏ Selected when $A_1=1, A_0=1$
- ⏏ Mode selection word
 - ⏏ Input/output modes




- ⏏ BSR mode




Select Input/output Modes

⌘ Input/output modes

 


Select Input/output Modes

⌘ Input/output modes

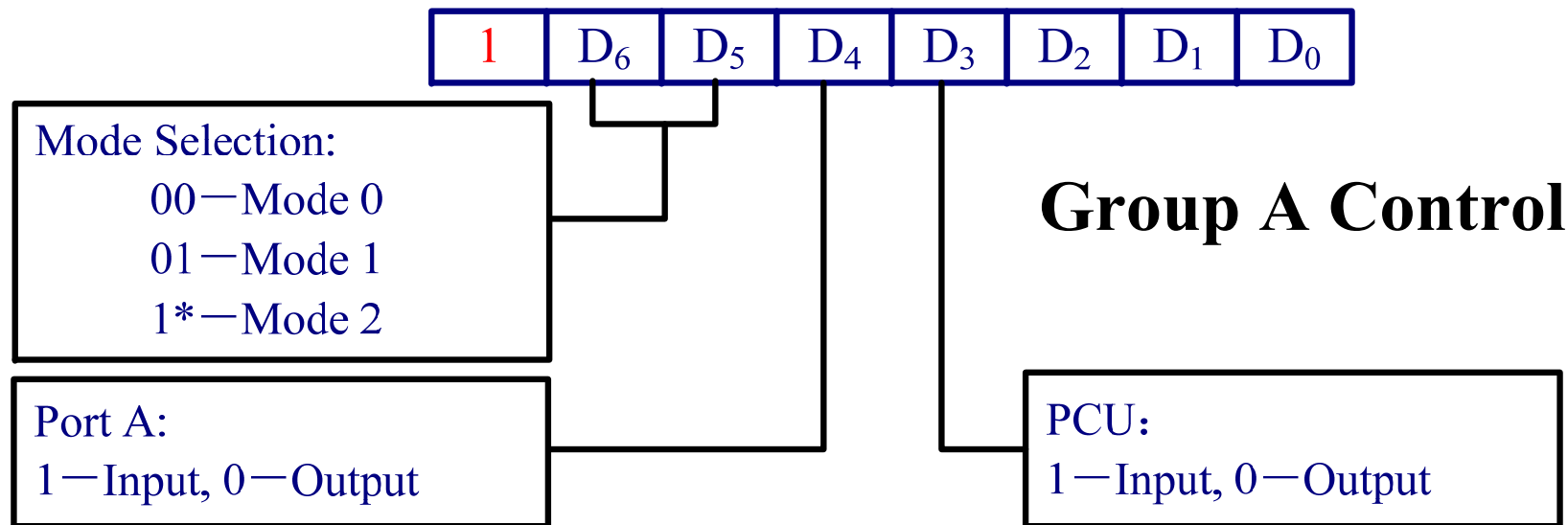

Select Input/output Modes

⌘ Input/output modes

 

Select Input/output Mode Examples

- ⌘ 1. Write ASM instructions for setting the 8255 in simple I/O mode with PA and PB being output port and PC being input port.


```
MOV AL, 10001001B  
OUT CPORT, AL
```

- ⌘ 2. Assume that the address of the control register of the 8255 is 63H, give out the instructions that set up the 8255 in mode 0 where PA, PB and PCU are used as input ports and PCL is used as output port.

```
MOV AL, 10011010B  
OUT 63H, AL
```

Select BSR Mode

⌘ BSR Mode

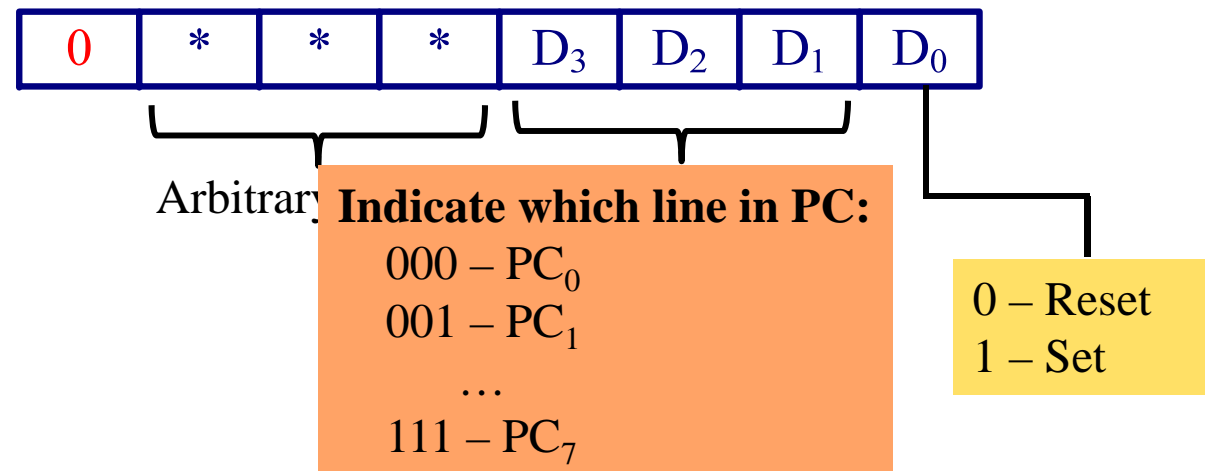

Select BSR Mode Examples

- ⌘ Assume PC is used as an output port which connects to 8 LED segments, now turn off the second LED segment with the rest unchanged (for LED segment, 1-on, 0-off).

```
In AL, CPORT  
AND AL, 11111101B  
OUT CPORT, AL
```

- ⌘ Using BSR mode instead:

```
MOV AL, 00000010B  
OUT ControlPORT, AL
```

Pros and cons?

Select BSR Mode Examples

- ⌘ Assume the address range for a 8255 PC is 60H~63H, PC₅ is outputting a low level, write code to generate a positive pulse.

```
MOV AL, 00001011B    ; set PC5 high level
OUT 63H, AL
MOV AL, 00001010B    ; set PC5 low level
OUT 63H, AL
```

Mode 0 in 8255

⌘ For simple input/output scenario

- ☑ No handshaking needed
- ☑ Any port of PA, PB and PC (PCU, PCL) can be programmed as input or output port independently
- ☑ $PCU = PC_4 \sim PC_7$, $PCL = PC_0 \sim PC_3$
- ☑ CPU directly read from or write to a port using IN and OUT instructions
- ☑ Input data **not** latched, Output data latched
- ☑ E.g.,

$D_7=1$	0	0	*	*	0	*	*
---------	---	---	---	---	---	---	---

Mode 1 in 8255

⌘ For **handshake** input/output scenario

- ☑ PA and PB can be used as input or output ports
- ☑ PCU = PC₃ ~ PC₇, used as handshake lines for PA
- ☑ PCL = PC₀ ~ PC₂, used as handshake lines for PB
- ☑ Both input and output data are latched

Mode 1: As Input Ports

⌘ $PC_3 \sim PC_5$ and $PC_0 \sim PC_2$ are used as handshake lines for **PA** and **PB**, respectively



☒ **~STB**: the strobe *input* signal from input device loads data into the port latch

☒ **IBF**: Input Buffer Full *output* signal to input device indicates that the input latch contains information

☒ **INTR**: Interrupt request is an output to CPU that requests an interrupts


⌘ **PC₆** and **PC₇** can be used as separate I/O lines for any purpose

⌘ **INTE**: the interrupt enable signal is neither an input nor an output; it is an internal bit programmed via the PC_4 (port A) or PC_2 (port B); 1-allowed, 0-forbidden

  


Mode 1: As Input Ports

⌘ Control register

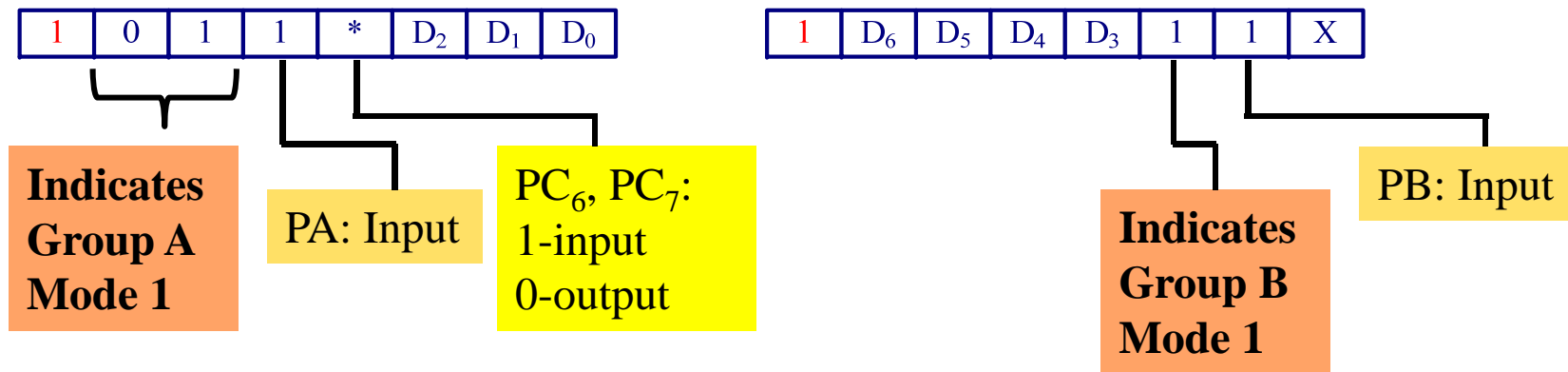

⌘ PC stores all status information


 


Timing in Mode 1 Input

- ⌘ Input device first puts data on $PA_0 \sim PA_7$, then activates $\sim STB_A$, data is latched in Port A;
- ⌘ 8255 activates IBF_A which indicates the device that the input latch contains information but CPU has not taken it yet. So device cannot send new data until IBF_A is cleared;
- ⌘ When both IBF_A and $INTE_A$ are active, 8255 activates $INTR_A$ to inform CPU to take data in PA by interruption;
- ⌘ CPU responds to the interruption and read in data from PA, clear $INTR_A$ signal;
- ⌘ After CPU finishes reading data from PA, the IBF_A signal is cleared;


Mode 1: As Output Ports

- ⌘ PC_3, PC_6, PC_7 and $PC_0 \sim PC_2$ are used as handshake lines for **PA** and **PB**, respectively
 - ☒ $\sim OBF$: Output buffer full is an *output* signal that indicates the data has been latched in the port
 - ☒ $\sim ACK$: The acknowledge *input* signal indicates that the external device has taken the data
 - ☒ **INTR**: Interrupt request is an output to CPU that requests an interrupts
- ⌘ **PC₄** and **PC₅** can be used as separate I/O lines for any purpose
- ⌘ **INTE**: the interrupt enable signal is neither an input nor an output; it is an internal bit programmed via the PC_4 (port A) or PC_2 (port B); 1-allowed, 0-forbidden

  


Mode 1: As Output Ports

⌘ Control register

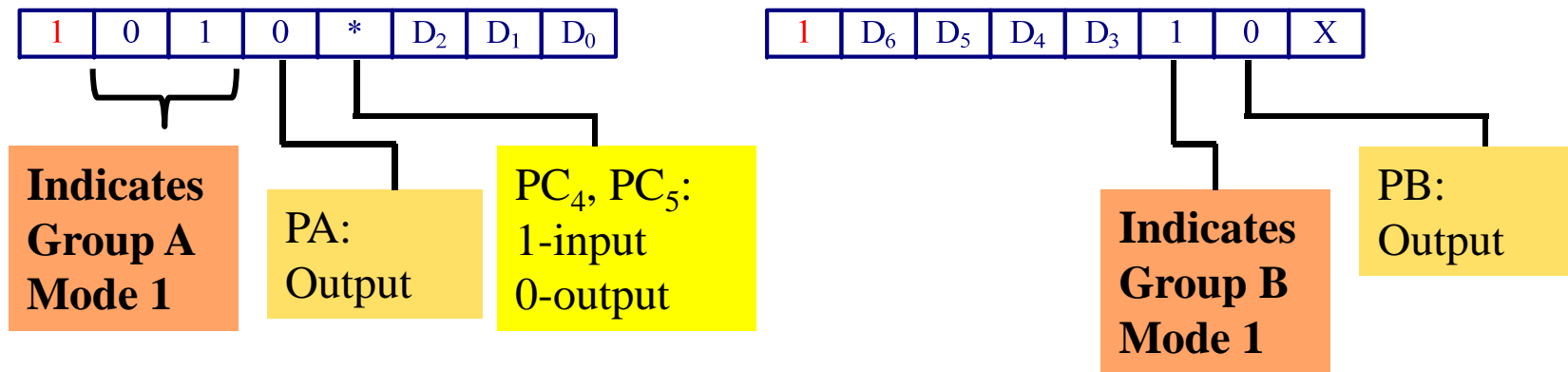

⌘ PC stores all status information

 

Timing in Mode 1 Output

- ⌘ If INTR_A active, CPU carries out OUT instruction which writes data to PA and clears the INTR_A signal;
- ⌘ When data has been latched in PA, 8255 activates $\sim\text{OBF}_A$ which informs the output device to pick up data;
- ⌘ After the output device has taken the data, it sends $\sim\text{ACK}_A$ signal to 8255 which indicates that the device has received the data, and also makes $\sim\text{OBF}_A$ go high, indicating CPU can write new data to 8255;
- ⌘ When $\sim\text{OBF}_A$, $\sim\text{ACK}_A$ and INTE_A are all high, 8255 sends an INTR_A to inform CPU to write new data to PA by interruption.


Mode 2 in 8255

⌘ For **bidirectional handshake** input/output scenario

- ☑ Only PA can be used as *both input and output port*
- ☑ PCU=PC₃~PC₇, used as handshake lines for PA
- ☑ Both input and output data are latched


Mode 2: As Input & Output Port

- ⌘ $PC_3 \sim PC_7$ are used as handshake lines for PA
- ⌘ $\sim OBF_A, \sim ACK_A, IBF_A, \sim STB_A, INTR_A$
- ⌘ $PC_0 \sim PC_2$ can be used as separate I/O lines for any purpose, or as handshake lines for PB

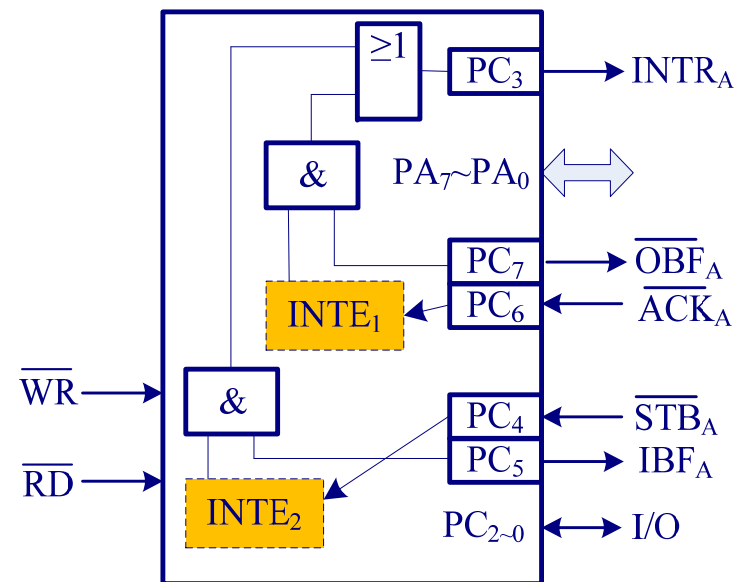


Mode 2: As Input & Output Port

⌘ Control register

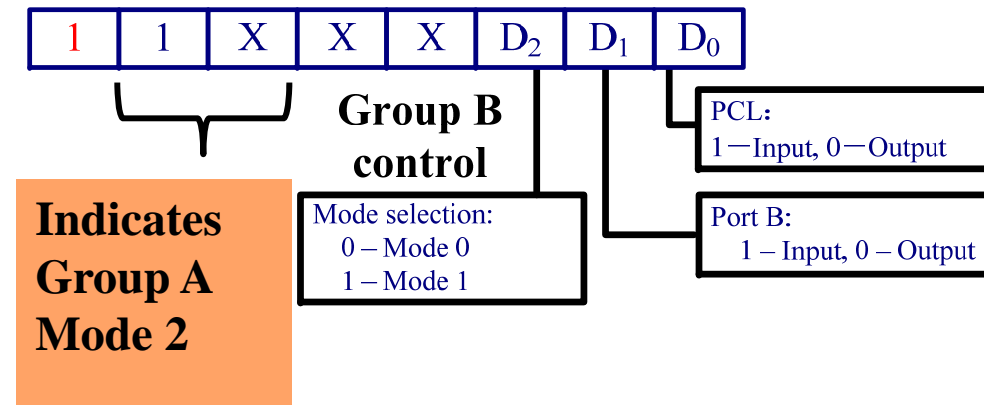

⌘ PC stores all status information

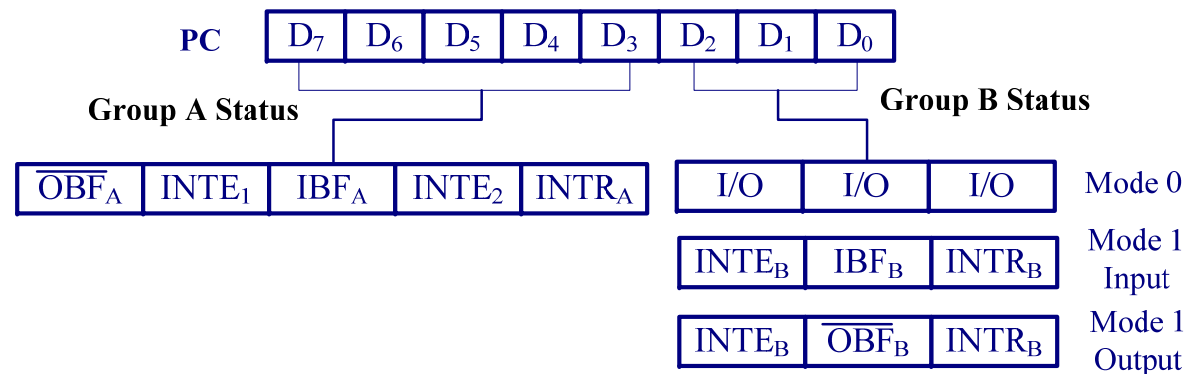



Polling vs. Interruptions

- ⌘ In Mode 1 and 2, PC stores status of Group A and/or Group B
- ⌘ By reading from PC using IN instruction, you can use polling method to check the state of I/O devices

Programming with 8255

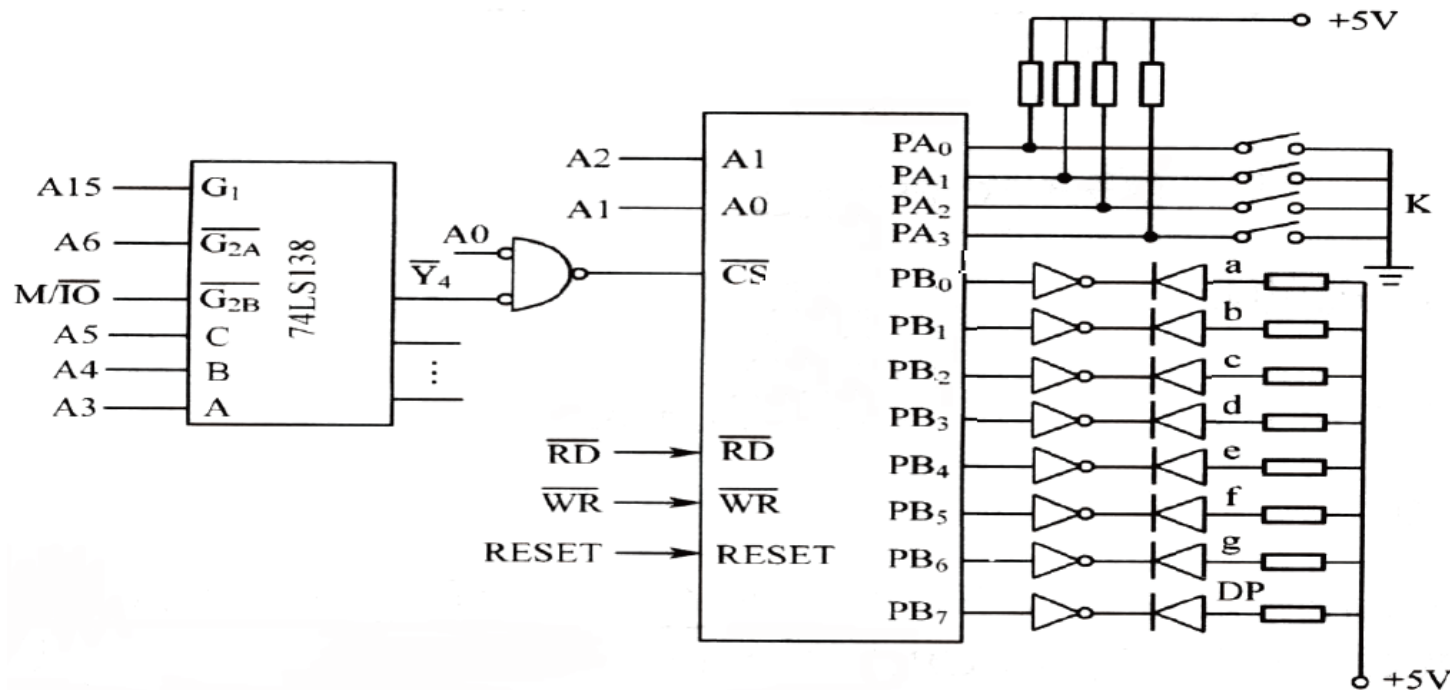- ⌘ As shown in the fig, PA and PB of the 8255 are working in mode 0. PA used as input port connects to 4 switches, and PB used as output port connects to a 7-segment LED. Write a program to display a hex digit that the switches can represent.



 

Address Decoding

⌘ What are the addresses of ports and the control register?

A ₁₉	A ₁₈	A ₁₇	A ₁₆	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
0	0	0	0	1	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0

⌘ PA : 8020H

⌘ PB : ?

⌘ PC : ?

⌘ CR : ?

A Solution Program

```
A_PORT EQU 8020H
B_PORT EQU 8022H
C_PORT EQU 8024H
CTRL_PORT EQU 8026H

DATA SEGMENT
    TAB1 DB C0H, F9H, C4H, ..., 0DH
DATA ENDS

CODE SEGMENT
    ASSUME CS:CODE, DS:DATA
START: MOV AX, DATA
        MOV DS, AX
```

A Solution Program

```
MOV AL, 90H      ; Set up the mode of 8255
MOV DX, CTRL_PORT
OUT DX, AL
ADD1: MOV DX, A_PORT
    IN  AL, DX    ; read the status of switches
    AND AL, 0FH
    MOV BX, OFFSET TAB1
    XLAT
    MOV DX, B_PORT ; output to LED
    OUT DX, AL

    MOV CX, 0600H ; delay for lighting the LED
ADD2: LOOP ADD2
    JMP ADD1
CODE ENDS
    END START
```